

addiu logic instruction:

implementation:

schematic

jr : R-type instruction with funct=8

lbu : I-TYPE instruction with OPCODE = 6'b(100100)

Load half and load byte

introduction:

Recipe:

Items/Pins:

implementation:

schematic:

Code:

Reference:

Store half and store byte

introduction:

implementation:

schematic:

Code:

Reference:

Shift Word Left Logical Variable

introduction:

machine code

assembly format

operation

implentaion

controls r-type_controls

code changes:

alu.sv

aludec.sv

schematic:

Reference:

Shift Right Logical:

introduction:

Recipe:

implementation:

schematic:

addiu logic instruction:

The **addiu** instruction does a addition of two 32-bit . At run time the 16-bit immediate operand is sign extended to make it a 32-bit operand. the following is a machine code description for addiu:

```
addiu $rt, $rs, immed
```

implementation:

this design is based on the fact that addiu is identical to addi with different overflow behavior


opcode

control

000101

10010000000000000000

schematic

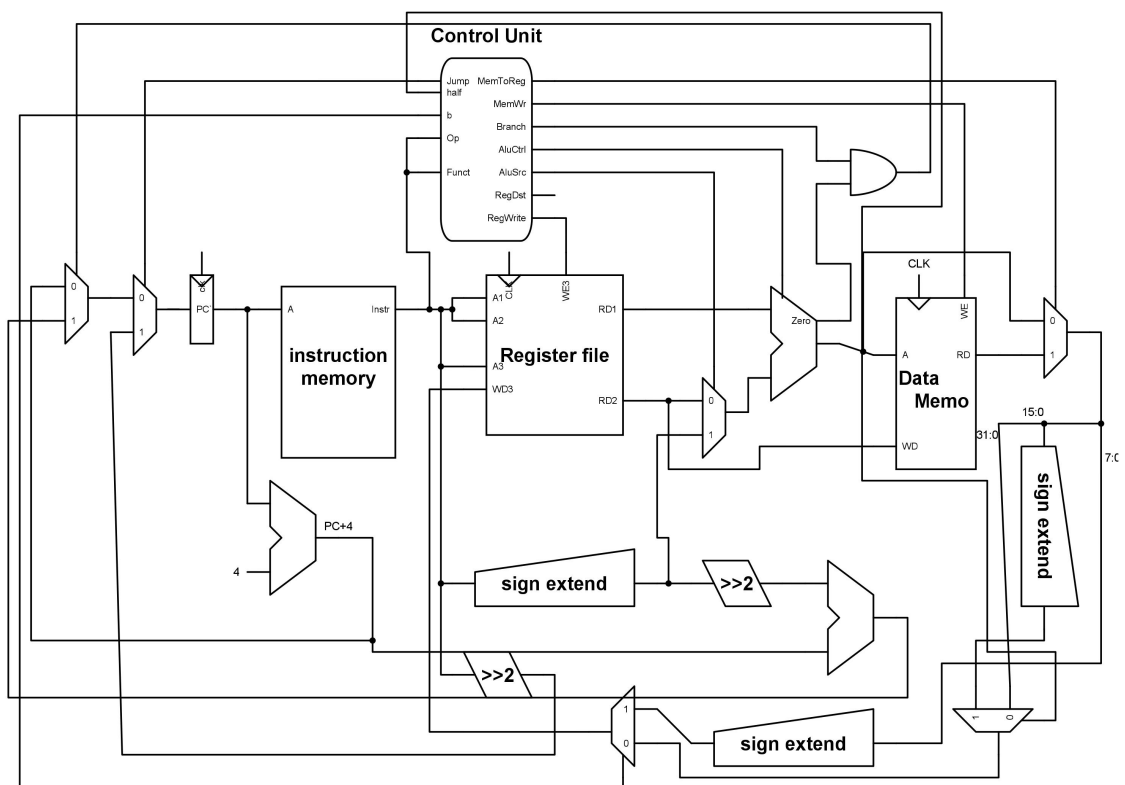

jr : R-type instruction with funct=8

```
jr $rs
```

example:

```
jr $r7  
pc=$r7
```

- puts rs : instr[25:21] value inside PC reg to perform unconditional jump via reg value
- jr signal added to controller and is assigned to 1 when funct=8 and opcode =8
- implementation :
 - MUX with four selectors with inputs (PC+4,PC Branch,srca,zeros) and selectros {pcsrc,jr}
 - srca in code is RD1 in diagram(value of rs)

jr	pcsrc	output
0	0	PC
0	1	PC branch
1	0	srca
1	1	zeros

lbu : I-TYPE instruction with OPCODE = 6'b(100100)


```
lbu $rt, imm($rs)
```

example:

```
lbu $r7 82($r3)
r7=memory[82/4+r3]
r3 is base address and imm is offest
```

- lbu signal added to control unit and is assigned to 1 when OPCODE = 6'b(100100) to write value at base address rs with offest imm
- implementation :
 - MUX with four selectors with inputs (alu output ,output of data memory,output of data memory [7:0],zeros) and selectros {memtoreg,lbu}

memtoreg	lbu	output
0	0	alu output
0	1	Data memory
1	0	zeroext(Data memory from [7:0])
1	1	zeros

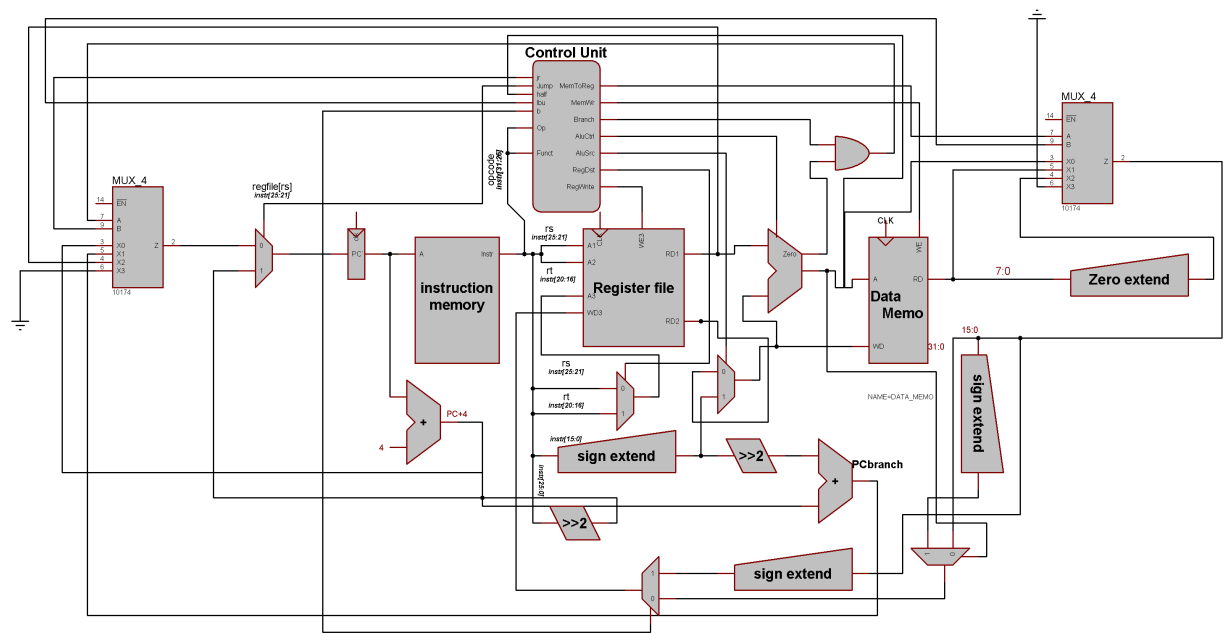

Load half and load byte

introduction:

a "Load half" and "Load byte" implementation using MIPS micro-architecture was built upon Harris design in their book (reference)

```
lh $storeReg imm($regRefearingToMemAddress)
```

```
lb $storeReg imm($regRefearingToMemAddress)
```

the following is a machine code description for lh and lb

```
lh: 100001 $regRefearingToMemAddress $storeReg iiii iiii iiii iiii
lb: 100000 $regRefearingToMemAddress $storeReg iiii iiii iiii iiii
```

Recipe:

Items/Pins:

1. pin_b (byte) : used as a selector for mux[2]
2. half (half-word) : used as a selector for mux[1]
3. mux[1] (multiplexer): a multiplexer provide an option to full word or half word
4. mux[2] (multiplexer): a multiplexer provide an option to mux[1] or one byte

implementation:

this design is based on the fact that lw was already implemented and working well so why not to reuse it? at the output of **MemToReg** multiplexer (lw's output) i've used two multiplexers mux[1] and mux [2]


mux[1] will chose from the full word (32-bit) and a sign-extended half word $\{16\{\text{halfword}[15]\}, \text{halfword}[15:0]\}$ using **half pin** as a controller

option (half pin)	operation
0	output of mux[1] equals the full word
1	output of mux[1] equals half of the word

mux[2] will chose from mux[1] output and a sign-extended one byte $\{24\{8\text{-bits}[7]\}, 8\text{-bits}[7:0]\}$ using **half pin** as a controller

option (b pin)	operation
0	output of mux[2] equals mux[1]
1	output of mux[2] equals sign extended one byte

schematic:

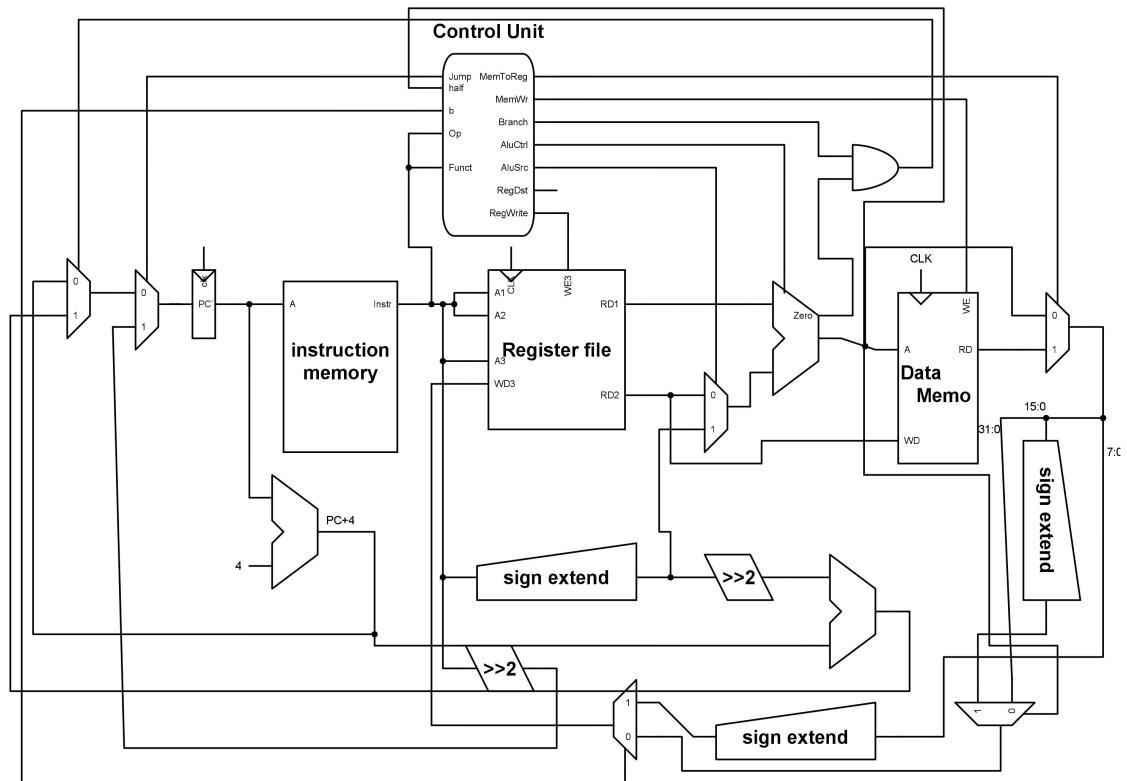

Code:

referring to the diff [file](#) to make a quick review to what i've changed/added

Reference:

Digital design and computer architecture by David and Sarah Harris

Store half and store byte

introduction:

a "store half" and "store byte" implementation using MIPS micro-architecture was built upon Harris design in their book (reference)

```
sh $ Registering value imm($regRefearingToMemAddress)
```

sb \$Registering value imm(\$regRefearingToMemAddress)

the following is a machine code description for sh and sb

```
sh: 101001  $regRefearingToMemAddress $storeReg iiiiii iiiiii
sb: 101000  $regRefearingToMemAddress $storeReg iiiiii iiiiii
```


implementation:

this design is based on the fact that sw was already implemented and working well so why not to reuse it? at the controller we make the **MemWr pin** 2 bits and **WE pin** also 2 bits,

in swthe alu result is address [32 bit] of the word and to move to the next word we sift the address left twice to add 4 so we always have 2 bits is **00** , we use this two bits to determined which number of bits in data memory to put the value of **reg** according to the following table :

option (WE pin)	operation
0 0	don't care
0 1	store word ,RAM[a[31:2]] <= wd;
1 0	store half word , {a[1],4'b0000} uses the second LSB as an indeicator to the upper or lower word starting point which is an intuitive approuch to reach the half word
1 1	store byte , {a[1:0],3'b000} uses the first and second LSB as an indeicator to the specified byte starting point which is an intuitive approuch to reach the byte

schematic:

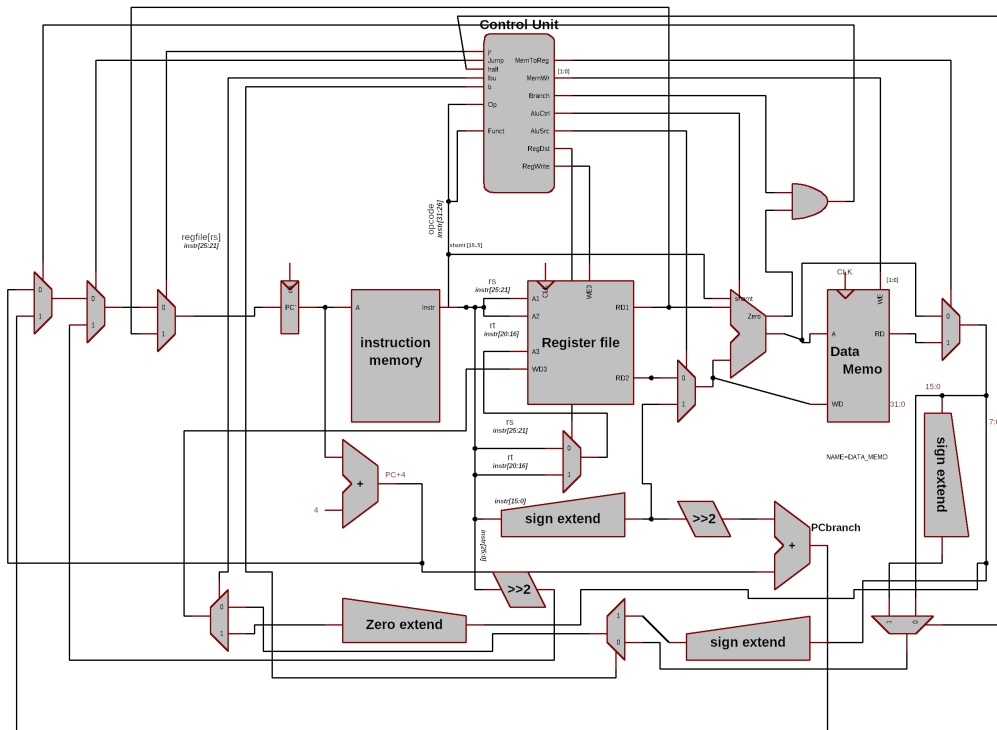

Code:

refearing to the diff [file](#) to make a quick review to what i've changed/added

Reference:


Digital design and computer architecture by David and Sarah Harris

Shift Word Left Logical Variable

introduction:

slv an (R type) instruction for shifting left a word by variable number

machine code

 

opcode	function
000000	000100

assembly format

```
sllv rd, rs, rt
```

operation

sllv would shift the value in reg(rs) ,by a number stored in low five bits in reg(rt),saving result in reg(rd)

implentaion

- add sllv operation in alu

controls *r-type_controls*

signal	value
REgWrite	1
RegDST	0
ALUSrc	11
Branch	0
MemWrite	0
MemtoReg	0
Jump	0
jr	0

signal	value
aluop	1111
ne	0
half	0
b	0
lbu	0
link	0

code changes:

alu.sv

add shift left operationg


```
y = b << a[4:0]
```

aludec.sv

chage the alucontrol to sllv

function	alucontrol
000100	< sllv operation >

schematic:

 

Reference:

[MIPS® Architecture for Programmers set manual 2016 pg377](#)

Shift Right Logical:

introduction:

MIPS also has a **shift right logical** instruction. It moves bits to the right by a number of positions less than 32. The high-order bit gets zeros and the low-order bits are discarded.

If the bit pattern is regarded as an unsigned integer, or a positive two's comp. integer, then a right shift of one bit position performs an integer divide by two. A right shift by N positions performs an integer divide by 2^N .

the following is a machine code description for Srl:

```
srl $rs $rt shift
```

Recipe:

mux[] (multiplexer): It would select Read data 1(rs) if we're not doing a shift operation, and it would select(rt) if we are doing a shift operation.

branch Instruction: we would need to branch Instruction[10:6] (the shift amount) off of Instruction[15:0], and Instruction[10:6] would then be fed into the other port of the ALU

implementation:

option (shift)	operation
0	output of mux[1] equals not doing a shift
1	output of mux[1] equals doing a shift operation.

schematic:

